

Patt & Patel, Problem 3.24, Page 89

- a. What is the output of the circuit?
 - When $X = 0$, $S =$
 - When $X = 1$, $S =$

- b. Modify the circuit (small adjustments only) so that
 - When $X = 0$, $S = A + B$
 - When $X = 1$, $S = A - B$

Figure 3.39, page 89

